

Questions



2.10 Given The Boolean Functions F_1 & F_2 show that

- (a) The Boolean Function $E = F_1 + F_2$ Contains the sum of the minterms of F_1 & F_2

$$F_1 = \sum m_{1i} = (m_{1,1} + m_{1,2} + \dots)$$

$$F_2 = \sum m_{2i} = (m_{2,1} + m_{2,2} + \dots)$$

$$F_1 + F_2 = \sum m_{1i} + \sum m_{2i}$$

$$= \sum (m_{1i} + m_{2i}) \neq$$

- (b) The Boolean Function $G = F_1 F_2$ Contains only the minterms that are common to F_1 & F_2 .

$$F_1 F_2 = \sum m_i \sum m_j$$

where $m_i m_j = 0$ if $i \neq j$

$$m_i m_j = 1 \text{ if } i = j$$

[2.16] The logical sum of All minterms of a Boolean Function of n Variables is $\underline{\underline{1}}$

a) prove The previous statement of $n=3$

Variables $n=3$

for Ex: A, B, C

A	B	C	F
0	0	0	$A'B'C'$
0	0	1	$A'B'C$
0	1	0	$A'B'C'$
0	1	1	$A'B'C$
1	0	0	$A'B'C'$
1	0	1	$A'B'C$
1	1	0	$A'BC'$
1	1	1	$A'BC$

$$F = A'B'C + A'B'C + AB'C + A'BC + A'B'C + A'B'C + ABC' + ABC$$

$$= A'(B'C + B'C + BC + BC) + A(BC' + BC + B'C + BC)$$

$$= (B'C + B'C + BC + BC)(A + A)$$

$$= B'C + B'C + BC + BC$$

$$= \bar{B}(C' + C) + B(C' + C)$$

$$= \bar{B} + B = 1 \neq 0$$

[2.17] obtain the Truth Table of the following functions & Express each function in Sum of Minterms & product of Maxterms form:

a) $(xy+z)(y+xz)$

x	y	z	xy	$xy+z$	xz	$y+xz$	$(xy+z)(y+xz)$
0	0	0	0	0	0	0	0 $\rightarrow m_0$
0	0	1	0	1	0	0	0 $\rightarrow m_1$
0	1	0	0	0	0	1	0 $\rightarrow m_2$
0	1	1	0	1	0	1	1 $\rightarrow m_3$
1	0	0	0	0	0	0	0 $\rightarrow m_4$
1	0	1	0	1	1	1	1 $\rightarrow m_5$
1	1	0	1	1	0	1	1 $\rightarrow m_6$
1	1	1	1	1	1	1	1 $\rightarrow m_7$

* Sum of Minterms:

$$F(x, y, z) = \sum (3, 5, 6, 7)$$

* Product of Maxterms:

$$F(x, y, z) = \prod (0, 1, 2, 4)$$

$$\boxed{b} (x+y')(y'+z)$$

	x	y	z	y'	$x+y'$	$y'+z$	$(x+y')(y'+z)$
0	0	0	0	1	1	1	1
0	0	1	1	1	1	1	1
0	1	0	0	0	0	0	0
0	1	0	0	1	1	0	0
1	0	0	1	1	1	1	1
1	0	1	1	1	1	1	1
1	1	0	0	1	1	0	0
1	1	0	1	1	1	1	1
1	1	1	1	1	1	1	1

* Sum of Minterms:

$$F(x,y,z) = \sum (0, 1, 4, 5, 7)$$

* Product of Maxterms

$$F(x,y,z) = \prod (2, 3, 6)$$

$$\boxed{C} x'y + wx'y + wy'z + w'y$$

	w	x	y	z	$x'z$	$wx'y$	wyz	$w'y$	F
0	0	0	0	0	0	0	0	1	1 m ₀
0	0	0	1	1	0	0	0	1	1 m ₁
0	0	1	0	0	0	0	0	0	0 m ₂
0	0	1	1	1	0	0	0	1	1 m ₃
0	1	0	0	0	0	0	0	1	1 m ₄
0	1	0	1	0	0	0	0	0	0 m ₅
0	1	1	0	0	0	0	0	0	0 m ₆
0	1	1	1	0	0	0	0	0	0 m ₇
1	0	0	1	1	0	0	0	0	0 m ₈
1	0	1	1	1	0	0	0	0	1 m ₉
1	1	0	0	0	0	1	1	0	1 m ₁₀
1	1	1	0	1	1	0	0	0	1 m ₁₁
					1	0	0	0	0 m ₁₂
					1	0	1	0	0 m ₁₃
					1	1	0	1	1 m ₁₄
					1	1	1	0	0 m ₁₅

* Sum of Minterms:

$$F(w,x,y,z) = \sum (0, 1, 3, 4, 5, 9, 10, 11, 14)$$

* Product of Maxterms:

$$F(w,x,y,z) = \prod (2, 6, 7, 8, 12, 13)$$

d) $(xy + yz' + x'z)(x+z)$

x	y	z	xy	yz'	$x'z$	$(xy + yz' + x'z)$	$(x+z)$	F
0	0	0	0	0	0	0	1	0
0	0	1	0	1	0	1	1	1
0	1	0	0	0	1	1	0	0
0	1	1	0	1	1	1	1	1
1	0	0	0	0	0	0	1	0
1	0	1	0	0	1	1	0	0
1	1	0	1	0	1	1	1	1
1	1	1	1	1	1	1	1	1

* Sum of Minterms :

$$F(x, y, z) = \sum (1, 3, 6, 7)$$

* product of Maxterms :

$$F(x, y, z) = \prod (0, 2, 4, 5)$$

Q.19 Express the following function as a sum of minterms & as a product of maxterms

$$F(A, B, C, D) = BD + A'D + B'D$$

A	B	C	D	$B'D$	$A'D$	BD	$F = (A'D+B'D+BD)$
0	0	0	0	1	1	0	1
0	0	0	1	0	0	0	0
0	0	1	0	0	0	0	0
0	0	1	1	1	1	0	1
0	1	0	0	0	0	0	0
0	1	0	1	0	1	1	1
0	1	1	0	1	0	1	1
0	1	1	1	1	1	1	1
1	0	0	0	0	0	0	0
1	0	0	1	0	0	1	1
1	0	1	0	0	1	0	0
1	0	1	1	0	1	1	1
1	1	0	0	1	0	0	0
1	1	0	1	1	0	0	1
1	1	1	0	1	1	0	0
1	1	1	1	1	1	1	1

* Sum of Minterms :

$$F(A, B, C, D) = \sum (1, 3, 5, 7, 9, 11, 13, 15)$$

* product of Maxterms :

$$F(A, B, C, D) = \prod (0, 2, 4, 6, 8, 10, 12, 14)$$

2.20 Express the Complement of the Following Functions in sum of minterms Form.

a) $\bar{F}(A, B, C, D) = \sum(3, 5, 9, 11, 15)$

* $\bar{F}(A, B, C, D) = \prod(0, 1, 2, 4, 6, 7, 8, 10, 12, 13, 14)$

b) $F(x, y, z) = \prod(2, 4, 5, 7)$

* $F(x, y, z) = \sum(0, 1, 3, 6)$

2.21 Convert each of the following to other Canonical Form:

a) $F(x, y, z) = \sum(2, 5, 6)$

$\bar{F}(x, y, z) = \prod(0, 1, 3, 4, 7)$

b) $\bar{F}(A, B, C, D) = \prod(0, 1, 2, 4, 7, 9, 12)$

$F(A, B, C, D) = \sum(3, 5, 6, 8, 10, 11, 13, 14, 15)$

2.22 Convert each of the following Expressions into Sum of products

a) $(AB + C)(B + C'D)$

= $ABB + ABC'D + BC + CC'D$

= $AB(B + C'D) + BC$

= $AB(1 + C'D) + BC$

= $AB + BC$ ~~#~~

b) $x' + x(x+y')(y+z') \rightarrow x+yz$

= $(x' + x)[(x' + (x+y')) \cdot (y+z')]$

= $(x' + x+y')(x'+y+z')$

~~($x' + y'$) ($x' + y + z'$)~~

= $(x' + y + z')$ ~~#~~

2.24 Show that The dual of The exclusive - OR is Equal to its Complement:

X	Y	$F = X \oplus Y$	X	Y	$F = (X \oplus Y)'$
0	0	0	0	0	1
0	1	1	0	1	0
1	0	1	1	0	0
1	1	0	1	1	1

$$F = x'y + xy'$$

$$F' = (x'y + xy)' = (x+y)' \cdot (x'+y) \quad \cancel{\text{X}}$$

2.25 By substituting The Boolean Expression Equivalent of Binary Operations as Defined in Table 2.8

a) The inhibition operation is neither Commutative nor Associative.

* inhibition operator $I \rightarrow x \mid y$
 $y \text{ is not } x \text{ or } x \text{ is not } y$

$$(x \mid y) = xy' \neq (y \mid x) = yx'$$

$$\begin{aligned} (x \mid y) \mid z &= xy' \mid z \neq x(y \mid z) = x(yz)' \\ &= x(y' + z') \\ &= xy' + xz' \end{aligned}$$

b) The Exclusive-OR operation is commutative & associative.

* $(X \oplus Y) = xy' + x'y \quad \Rightarrow \text{Commutative}$
 $(Y \oplus X) = yx' + y'x$

* $(X \oplus Y) \oplus Z = X \oplus (Y \oplus Z) \quad \text{Associative}$

$$\begin{array}{lll} x=0 & (0 \oplus 1) \oplus 1 & = 0 \oplus (1 \oplus 1) \\ y=1 & 1 \oplus 1 & = 0 \oplus 0 \\ z=1 & 0 & = 0 \end{array}$$

2.26 Show that positive logic NAND Gate is a negative logic NOR Gate & vice versa

(positive) NAND

X	Y	$F = (X \cdot Y)'$
0	0	1
0	1	0
1	0	0
1	1	0

Nor (negative).

X	Y	$F = (X + Y)'$
0	0	1
0	1	0
1	0	0
1	1	0

Positive Gate

x	y	$F = (x \cdot y)$
L (0)	L (0)	H (1)
L (0)	H (1)	H (1)
H (1)	L (0)	H (1)
H (1)	H (1)	L (0)

Negative Gate

x	y	$F = (x + y)$
L (0)	L (0)	H (1)
L (0)	H (1)	L (0)
H (1)	L (0)	L (0)
H (1)	H (1)	L (0)

1)

NAND positive.

x	y	$F = (x \cdot y)$
0	0	1
0	1	1
1	0	1
1	1	0

NOR negative.

x	y	$Z = (x + y)$
0	0	1
0	1	0
1	0	0
1	1	0

NAND negative.


x	y	$F = (x \cdot y)$
1	0	1
0	1	1
1	0	1
1	1	0

NOR positive.


x	y	$F = (x + y)$
0	0	1
0	1	0
1	0	0
1	1	0

2.28 Write Boolean Expressions & Construct the Truth Tables Describing The outputs of the Circuits Described by the Following logic Diagrams

(a)

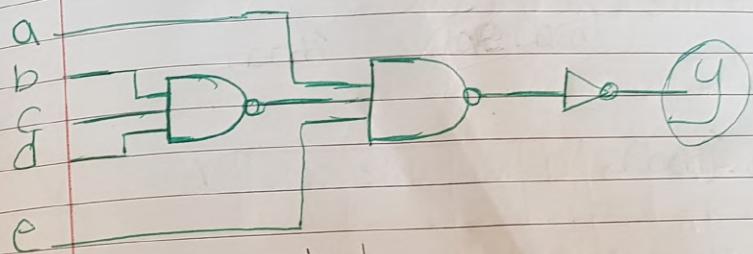

(b)

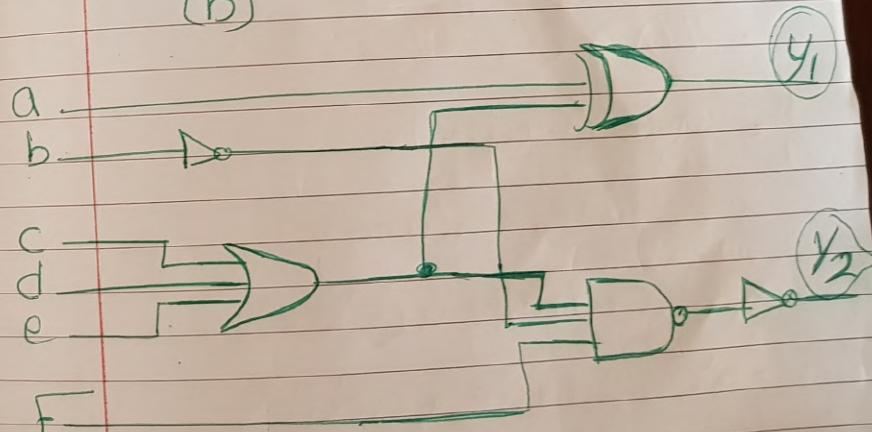

$$Y = ((a \cdot c \cdot (bcd)')')$$

$$\begin{aligned} &= a \cdot c \cdot (bcd)' \\ &= a \cdot c \cdot (b' + c' + d') \\ &= ab'c + ac'd + ad'c \end{aligned}$$

* Truth Table

a	b	c	d	e	ab'e	ac'e	ad'e	X
1	1	1	1	1	1	1	1	1
1	1	1	1	0	0	0	0	0
1	1	0	1	1	0	0	0	0
1	0	1	1	1	0	0	0	0
0	1	1	1	1	0	0	0	0
0	1	1	1	0	0	0	0	0
0	1	0	1	1	0	0	0	0
0	0	1	1	1	0	0	0	0

$$Y_1 = a \oplus (c+d+e)$$

$$\begin{aligned} &= a(c+d+e) + a(c+d+e)' \\ &= a(c+d+e) + a(c'd'e') \\ &= a'c + ad + a'e + ac'd'e' \end{aligned}$$

* Truth Table

a	b	c	d	e	a'c	a'd	a'e	a'c'd'e'	Y ₁
1	1	1	1	1	0	0	0	0	0
1	1	1	1	0	0	0	0	0	0
1	1	0	1	1	1	0	0	0	1
1	0	1	1	1	1	1	0	0	1
0	1	1	1	1	0	0	0	0	0
0	1	1	1	0	0	0	0	0	0
0	1	0	1	1	1	0	0	0	1
0	0	1	1	1	1	1	0	0	1

$$Y_2 = (((c+d+e) \cdot b' \cdot f)')$$

$$\begin{aligned} &= (c+d+e) \cdot b' \cdot f \\ &= b'c'f + db'f + b'cf \end{aligned}$$

* Truth Table

b	c	d	f	b'c'f	db'f	b'cf	Y ₂
1	1	1	1	1	1	1	1
1	1	1	0	0	0	0	0
1	0	1	1	0	0	0	0
0	1	1	1	0	0	0	0
0	1	1	0	0	0	0	0
0	0	1	1	0	0	0	0
0	0	0	1	0	0	0	0

Multiplexer



* Multiplexer:

Combinational Circuits That Select Binary Information From One of many inputs lines & Directs it To a Single output line.

- Selection lines used to Control Input lines.
- n selection used to select Input lines
- 2^n Inputs
- MUX \rightarrow (Multiplexer)

$$- \text{MUX } (4 \times 1) = (n \times 1)$$


↓ ↓
Inputs Outputs

Ex:

Mux (4×1)

Mux (8×1)

Mux (16×1)

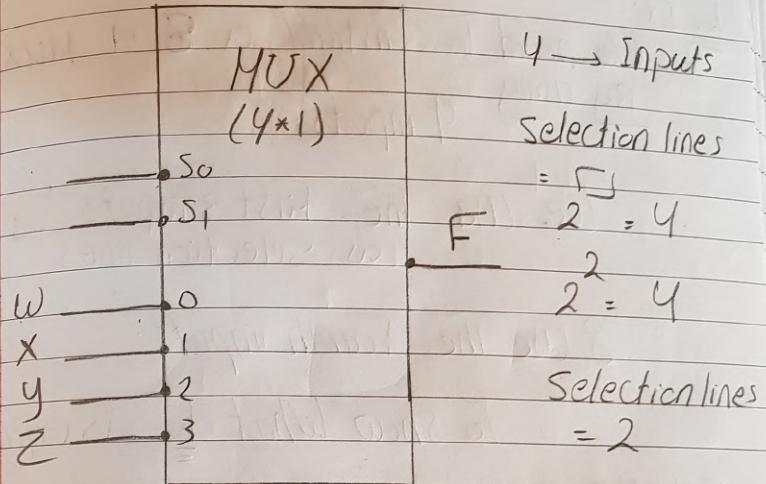

selection lines → output line.

S ₀	S ₁	F
0	0	w
0	1	x
1	0	y
1	1	z

العدد Selection lines ال عدد وحدات *

output line.

Number of Selection lines = $2^2 = 4$ → Inputs.

Ex: 4 inputs
 $2^2 = 4$ Selection lines = 2

For Ex:

We need To Construct a 8×1 Mux
By using 4 inputs

We use The First 3 inputs
as Selection lines

8 use The Fourth inputs

To show what \underline{F} is equal.

Selectors

x	y	z	w	F
0	0	0	0	0
0	0	0	1	1
0	0	1	0	0
0	0	1	1	1
0	1	0	0	0
0	1	0	1	1
0	1	1	0	1
0	1	1	1	0

$$F = w^1$$

x	y	z	w	F
0	0	1	0	0
0	0	1	1	1
0	1	0	0	0
0	1	0	1	1

$$F = w$$

x	y	z	w	F
0	1	0	0	0
0	1	0	1	1
0	1	1	0	1
0	1	1	1	0

$$F = 1$$

x	y	z	w	F
1	0	0	0	0
1	0	0	1	1
1	0	1	0	1
1	0	1	1	0

$$F = w^1$$

x	y	z	w	F
1	0	1	0	0
1	0	1	1	1
1	1	0	0	1
1	1	0	1	0

$$F = w$$

x	y	z	w	F
0	0	1	0	0
0	0	1	1	1
0	1	0	0	1
0	1	0	1	0

$$F = 1$$

x	y	z	w	F
1	1	0	0	0
1	1	0	1	1
1	1	1	0	1
1	1	1	1	0

$$F = w$$

Decoder

* Decoder.

Combinational Circuits that convert n input lines to 2^n outputs ~~or~~ lines.

- Decoder is

n -to- m line Decoder

inputs \downarrow outputs

$$m \leq 2^n$$

- For Ex:

DEC (3 * 8)

inputs \downarrow outputs

$$n=3$$

$$m=2^3=8$$

* Decoders with E (Enable) Inputs can be connected together to form large Decoder circuit.

When $E=0$ \rightarrow The Top (First) Decoder is Enabled & The other Decoder is Disabled

$E=1$ \rightarrow The Bottom Decoder is Enabled & The Top Decoder is Disabled.

Inputs			outputs							
X	y	Z	D ₀	D ₁	D ₂	D ₃	D ₄	D ₅	D ₆	D ₇
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0
0	1	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	1	0	0	0	0
1	0	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	0	0	0	1	0
1	1	0	0	0	0	0	0	0	1	0
1	1	1	0	0	0	0	0	0	0	1

Ex:


Construct 4×16 Decoder with Two
 3×8 Decoders.

$$- 4 \times 16 \quad n=4 \quad m=2^4 = 16 \\ \text{using}$$

Two Decoders 3×8

$$n=3 \quad m=2^3 = 8$$

- \underline{E} (Enable line)

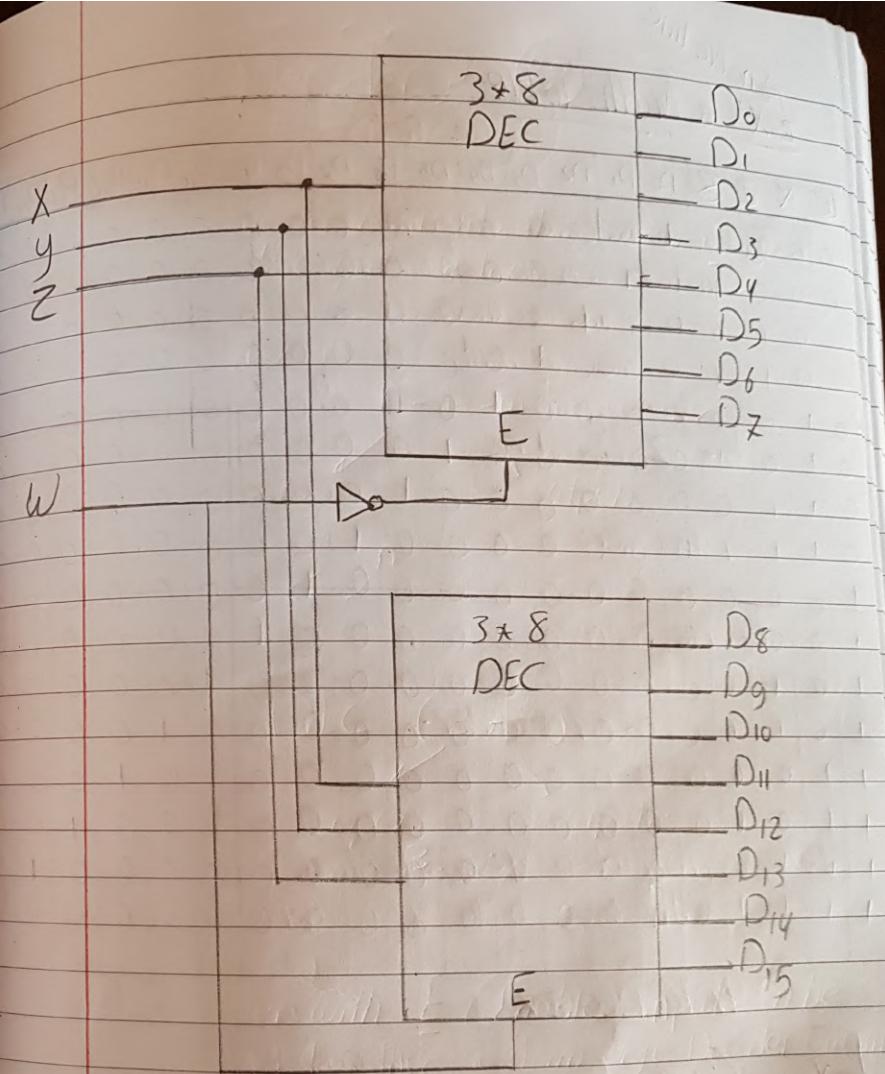

Enable line

Truth Table

Ex:

Construct 3×8 Decoder.

$$n = 3 \quad m = 2^3 = 8$$

8 * 3
DEC

DEC

D.

91

12

1

1

D

10

06

10

1

* Truth Table

Ch 4:

Questions

4.25

Construct a 5-to-32 line Decoder with Four 3-to-8 line Decoders. Use Block Diagram For The Components.

5*32 Decoder.

4 Decoders (3*8)

Enable

(is addressed)

2*4 Decoder.

4.26

Construct a 4-to-16 line Decoder with Five 2-to-4 Decoders with Enable.

4*16 Decoder

4 Decoders (2*4)


(4)

- Enable





1 Decoder (2*4).

4.25


A
B
C

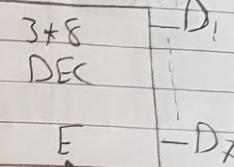

D
E

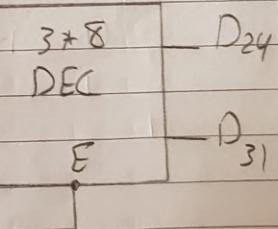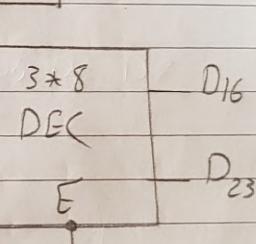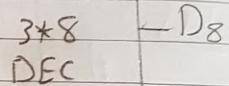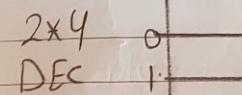

4.26

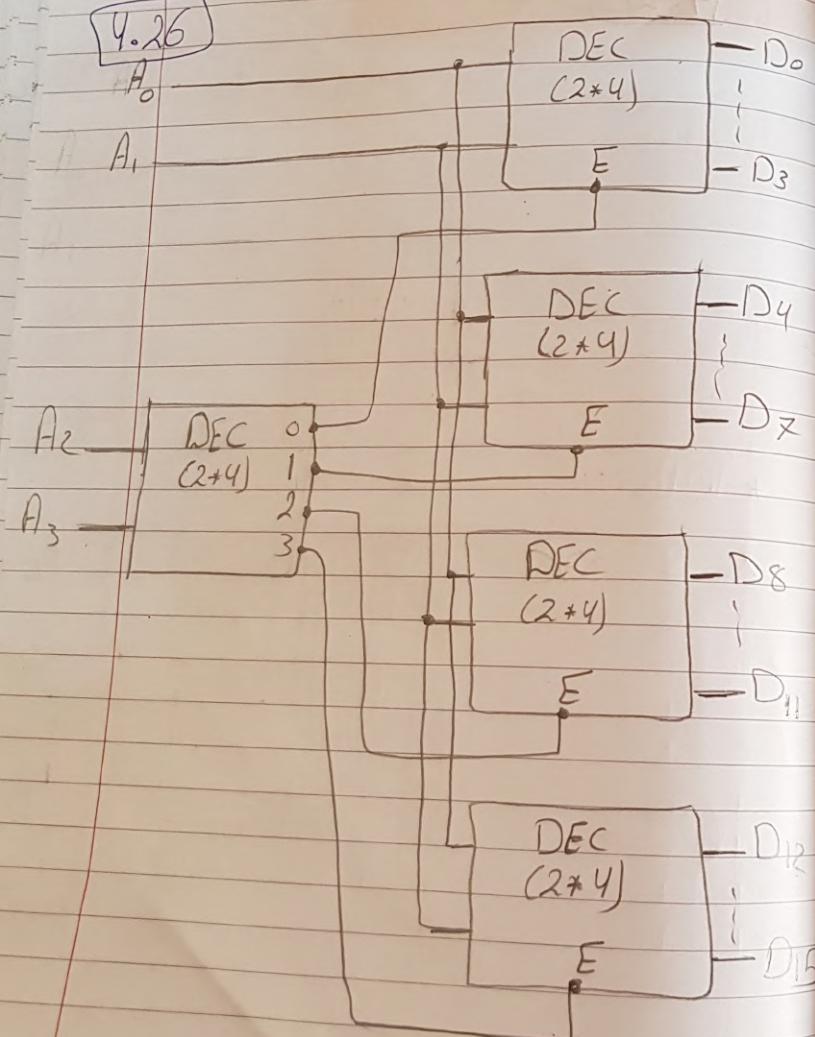

4.31


Construct 16*1 Multiplexer with Two 8*1 & 2*1 Multiplexer Use Block Diagrams

* 16*1 Multiplexer

$$\begin{cases} 2 \text{ MUX } (8 \times 1) \\ 1 \text{ MUX } (8 \times 1) \end{cases}$$

$$\begin{aligned} n &= 16 \\ \text{Selection lines} \\ \Rightarrow 2^4 &= 16 \\ S &= 4 \end{aligned}$$

* 2 MUX (2x1)

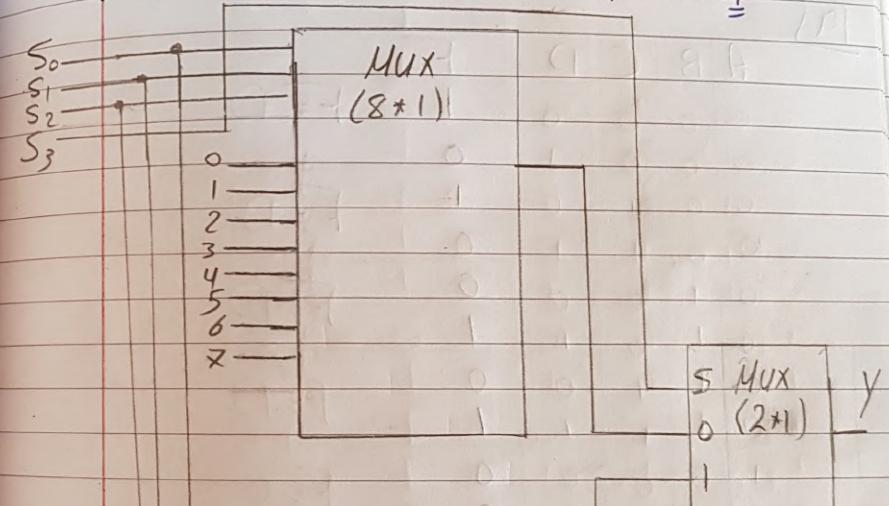

MUX 1
(8*1)

$$\begin{array}{c} 0 \\ 1 \\ 2 \\ 3 \\ 4 \\ 5 \\ 6 \\ 7 \end{array}$$

Q.32 Implement The Following Boolean Function
with a Multiplexer.

$$\bar{a} \bar{f}(A, B, C, D) = \sum(0, 2, 5, 7, 11, 14)$$

$$b) f(A, B, C, D) = \prod(3, 8, 12)$$


a)

A	B	C	D	F
0	0	0	0	1
0	0	0	1	0
0	0	1	0	1
0	0	1	1	0
0	1	0	0	0
0	1	0	1	1
0	1	1	0	0
0	1	1	1	1
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	1
1	1	0	0	0
1	1	0	1	0
1	1	1	0	1
1	1	1	1	0

8*1 Mux

8 inputs
3 selectors

$$2^3 = 8$$

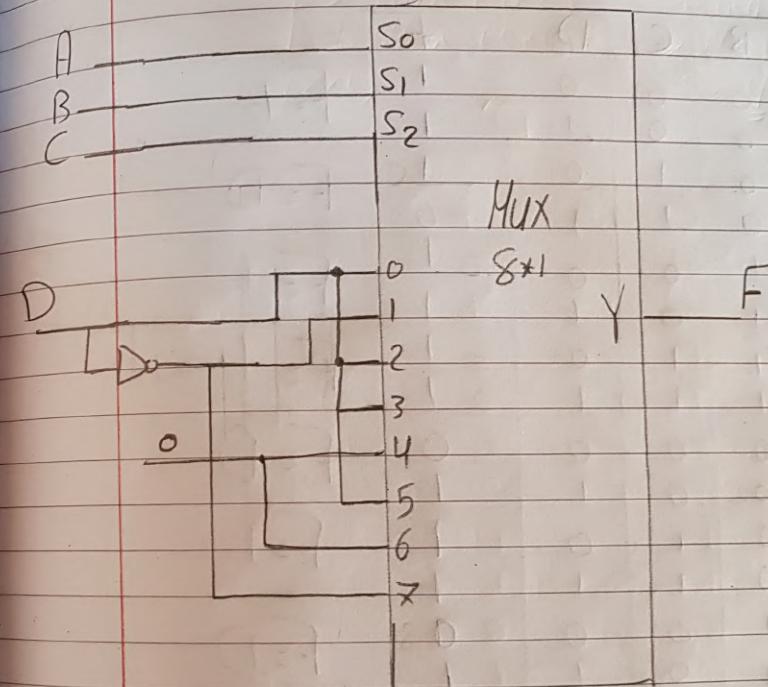

$$\boxed{b} \quad F = \overline{\prod} (3, 8, 12)$$

$$F = \sum (0, 1, 2, 4, 5, 6, 7, 9, 10, 11, \cancel{12}, 13, 14, 15)$$


A	B	C	D	F
0	0	0	0	1
0	0	0	1	1
0	0	1	0	1
0	0	1	1	0
0	1	0	0	1
0	1	0	1	1
0	1	1	0	1
0	1	1	1	1
1	0	0	0	0
1	0	0	1	1
1	0	1	0	1
1	0	1	1	1
1	1	0	0	0
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1

8*1 MUX

8 = inputs

8 = 2³

3 Selection lines

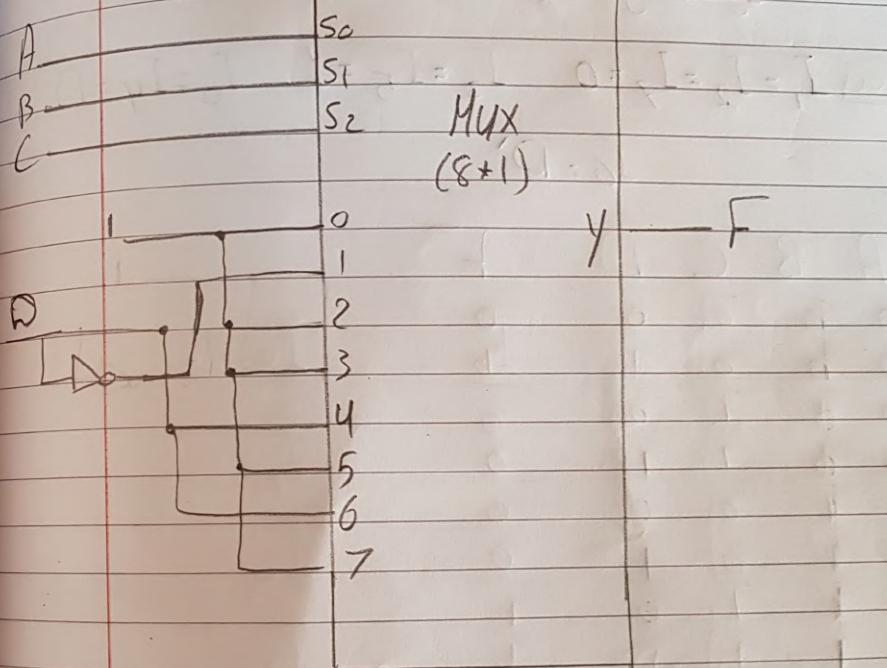

4.34 An 8*1 Multiplexer has inputs A, B & C connected to the selection inputs S_2, S_1 & S_0 respectively. The Data inputs I_0 through I_7 are as follows:

$$\text{a) } I_1 = I_2 = I_7 = 0 \quad I_3 = I_5 = 1 \quad I_0 = I_4 = D \\ I_6 = D'$$

A	B	C	D	F
0	0	0	0	0
0	0	0	1	1
0	0	1	0	0
0	0	1	0	0

$$I_0 = D$$

A	B	C	D	F
0	0	0	0	0
0	0	0	1	1
0	0	1	0	0
0	0	1	0	0

$$I_1 = 0$$

A	B	C	D	F
0	1	0	0	1
0	1	1	1	1
1	0	0	0	0
1	0	0	1	1

$$I_2 = 0$$

A	B	C	D	F
1	0	1	0	1
1	0	1	1	1
1	1	0	0	0
1	1	0	1	1

$$I_3 = 1$$

A	B	C	D	F
1	1	0	0	1
1	1	0	1	0
1	1	1	0	0
1	1	1	1	1

$$I_4 = D$$

A	B	C	D	F
1	0	1	0	1
1	0	1	1	0
1	1	0	0	0
1	1	0	1	1

$$I_5 = 1$$

A	B	C	D	F
1	1	0	0	1
1	1	0	1	0
1	1	1	0	0
1	1	1	1	1

$$I_6 = D'$$

A	B	C	D	F
1	1	0	0	1
1	1	0	1	0
1	1	1	0	0
1	1	1	1	1

$$I_7 = 0$$

* Determine The Boolean Function that The Multiplexer Implements.

$$F(A, B, C, D) = \sum(1, 6, 7, 9, 10, 11, 12)$$

$$\text{b) } I_1 = I_2 = I_7 = 0 \quad I_3 = I_7 = 1 \quad I_4 = I_5 = D \\ I_0 = I_6 = D'$$

A	B	C	D	F
0	0	0	0	1
0	0	0	1	0
0	0	1	0	0
0	0	1	0	0

$$I_0 = D'$$

A	B	C	D	F
0	0	1	1	0
0	0	1	1	0
0	0	1	0	0
0	0	1	0	0

$$I_1 = 0$$

A	B	C	D	F
0	1	0	0	1
0	1	0	1	1
0	1	1	0	0
0	1	1	0	0

$$I_2 = 0$$

A	B	C	D	F
1	0	0	0	0
1	0	0	1	1
1	0	1	0	0
1	0	1	0	0

$$I_3 = 1$$

A	B	C	D	F
1	0	0	0	0
1	0	0	1	1
1	0	1	0	0
1	0	1	0	0

$$I_4 = D$$

A	B	C	D	F
1	1	0	0	0
1	1	0	1	1
1	1	1	0	0
1	1	1	0	0

$$I_5 = D$$

A	B	C	D	F
1	1	1	0	0
1	1	1	0	0
1	1	1	1	1
1	1	1	1	1

$$I_6 = D'$$

A	B	C	D	F
1	1	1	0	0
1	1	1	0	0
1	1	1	1	1
1	1	1	1	1

$$I_7 = 1$$

$$f(A, B, C, D) = \sum (0, 6, 7, 9, 11, 12, 14, 15)$$